



DENEY RAPORU

Deney Adı	Transistor Amplifier Circuits
Deneyi Yaptıran Ar. Gör.	Melih Bilmez
Raporu Hazırlayan (İsim / Numara / Bölüm)	Ömer Malik Kalembaşı / 150180112 / Computer Engineering
Grup Numarası ve Deney Tarihi	C3/ March 24, 2021

Rapor Notu	Teslim Edildiği Tarih	Teslim Alındığı Tarih
	March 24, 2021	

Experiment 3.1.

Simulate the circuit shown in Fig.1. **BC847A should be used for BJT.**

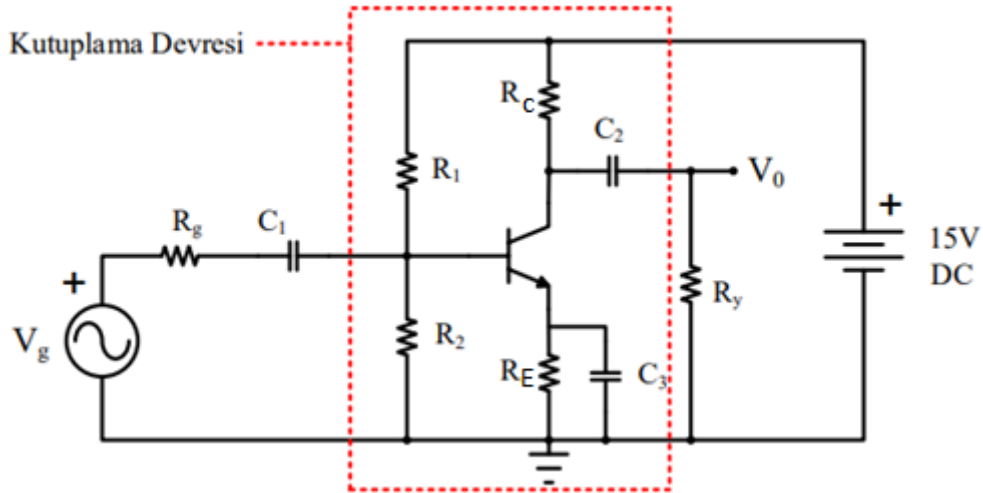


Figure 1. BJT Amplifier

Table 1. Values of components in circuit.

R_1	220 k Ω	R_g	10 k Ω
R_2	33 k Ω	R_y	12 k Ω
R_c	8.2 k Ω	$C_{1,2}$	4.7 μ F
R_E	1.2 k Ω	C_3	220 μ F

Table 2. Input Signal Parameter (V_g) for experiment 3.1.

Exp: 3.1 – V_g	
Type	Sine
Frequency	5 kHz
DC Offset	0V

Outputs:

1. Note the DC operating points.


```
* D:\itu cmpe\spring 20-21\ehb311\deney3\3_1lab.asc

--- Operating Point ---

V(c) :          7.13985      voltage
V(b) :          1.80684      voltage
V(e) :          1.15653      voltage
V(n001) :        15          voltage
V(n004) :      8.49214e-014    voltage
V(n003) :         0          voltage
V(n002) :      4.02688e-013    voltage
Ic(Q1) :      0.000958555      device_current
Ib(Q1) :      5.21625e-006      device_current
Ie(Q1) :     -0.000963771      device_current
I(C1) :      8.49214e-018      device_current
I(C2) :     -3.35573e-017      device_current
I(C3) :      2.54436e-016      device_current
I(Ry) :      3.35573e-017      device_current
I(Rg) :      8.49214e-018      device_current
I(Re) :      0.000963771      device_current
I(R2) :      5.47527e-005      device_current
I(Rc) :      0.000958555      device_current
I(R1) :      5.99689e-005      device_current
I(V2) :      8.49214e-018      device_current
I(V1) :     -0.00101852      device_current
```

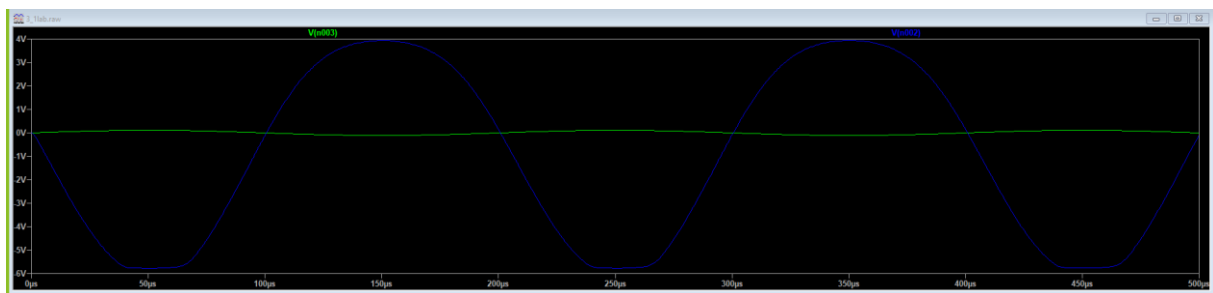
2. What is the V_g value at which clipping starts? Also, is there symmetrical clipping?

There is clipping, starts at $V_g=110\text{mV}$.




3. Plot the output voltage (V_o-t), input voltage (V_g-t) and (V_e-t). What is the voltage gain (V_o/V_g)?

$$3.7\text{V}/0.1\text{V} = 3$$

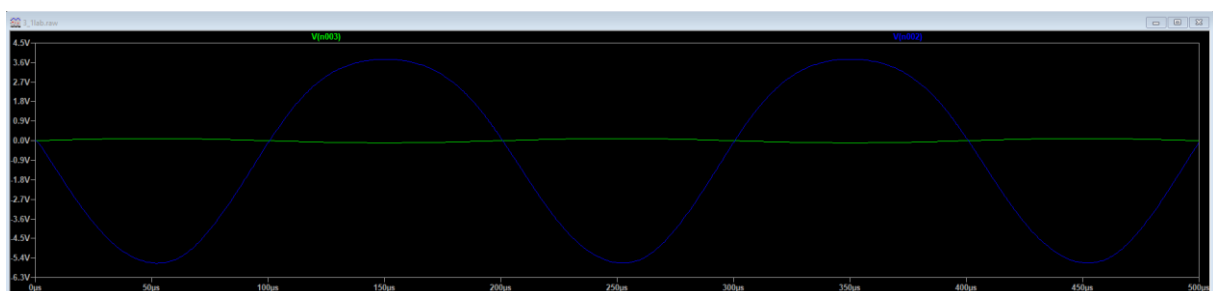

4. Remove the C_3 capacitor from circuit and repeat simulation. Plot the output voltage (V_o -t), input voltage (V_g -t) and (V_e -t). What is the voltage gain (V_o/V_g)?

$$282\text{mV}/100\text{mV} = 2.82$$

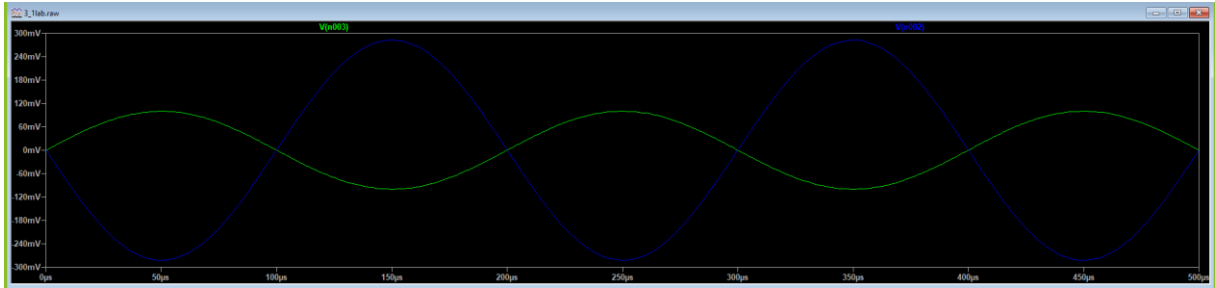

5. Explain the circuit and simulation results.

In AC operation, C_3 capacitor will be bypass; in DC biasing resistor R_e will work. When C_3 connected, performance gained.

Experiment 3.2.

Simulate the circuit shown in Fig.2. **BSP89 should be used for MOSFET.**

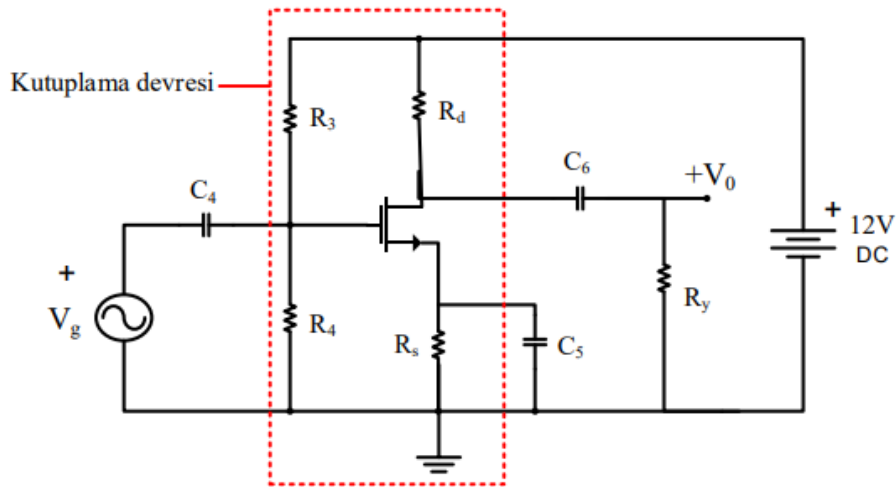


Figure 2. MOSFET Amplifier.

Table 4. Values of components in circuit.

R_3	820 k Ω	R_s	220 Ω
R_4	330 k Ω	R_y	10 k Ω
R_d	1 k Ω	$C_{4,5,6}$	1 μF

Table 5. Input Signal Parameter (V_g) for experiment 3.2.

Exp: 3.2 – V_g	
Type	Sine
Frequency	50 kHz
DC Offset	0V

Outputs:


1. Note the DC operating points.

```
* D:\itu cmpe\spring 20-21\ehb311\deney3\3_2lab.asc

--- Operating Point ---
V(n001) :      12          voltage
V(g) :       3.44348      voltage
V(d) :       4.15258      voltage
V(s) :       1.72643      voltage
V(n002) :     4.15258e-014 voltage
V(n003) :      0          voltage
Id(M1) :     0.00784742    device_current
Ig(M1) :    -1.14489e-010 device_current
Is(M1) :    -0.00784742    device_current
I(C4) :     3.44348e-018    device_current
I(C6) :    -4.15258e-018    device_current
I(C3) :     1.72643e-018    device_current
I(Ry) :     4.15258e-018    device_current
I(Rs) :     0.00784742    device_current
I(R4) :     1.04348e-005    device_current
I(Rd) :     0.00784742    device_current
I(R3) :     1.04348e-005    device_current
I(Vg) :     3.44348e-018    device_current
I(V1) :    -0.00785785    device_current
```

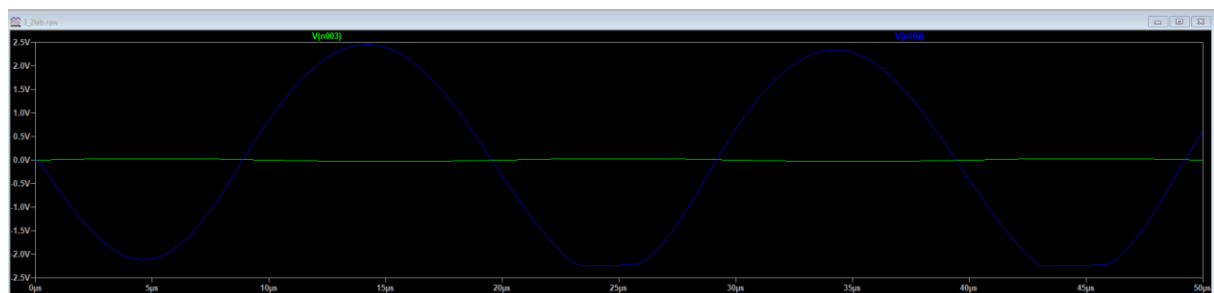
2. What is the V_g value at which clipping starts? Also, is there symmetrical clipping?

There is clipping, starts at $V_g=33\text{mV}$




3. Plot the output voltage (V_o-t) and input voltage (V_g-t). What is the voltage gain (V_o/V_g)?

$$V_o/V_g = 2.25/0.03 = 75$$

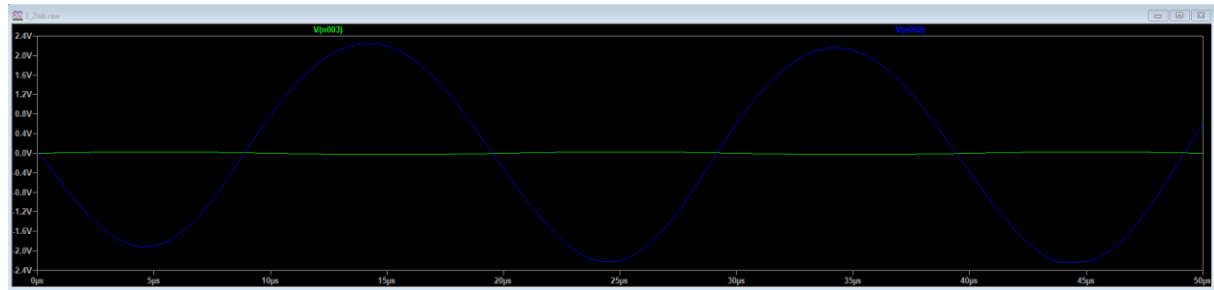

4. Remove the C_5 capacitor from circuit and repeat simulation. Plot the output voltage (V_o-t) and input voltage (V_g-t). What is the voltage gain (V_o/V_g)?

$$117\text{mV}/30\text{mV} = 3.9$$

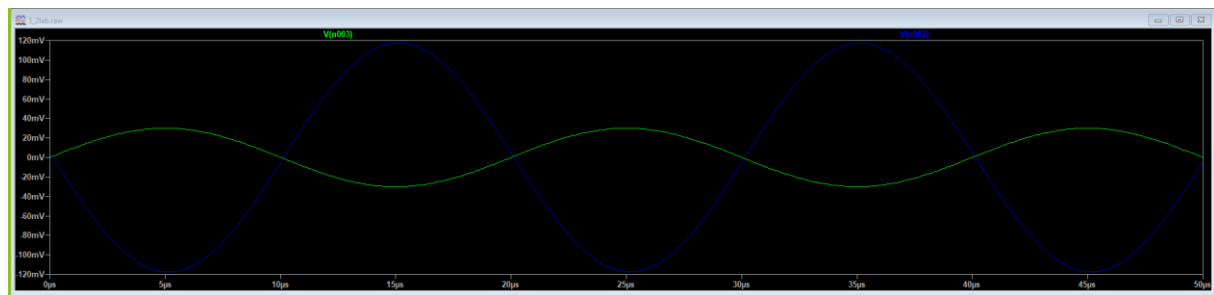

5. Explain the circuit and simulation results.

In AC operation, C_3 capacitor will be bypass; in DC biasing resistor R_s will work. When C_5 is connected, performance is gained.

Last Update: 30.10.2020